
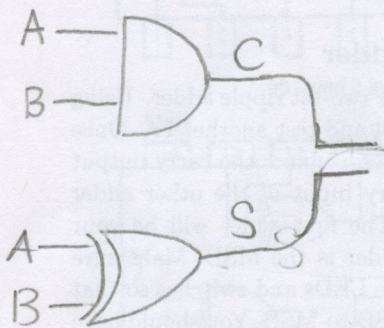



Circuit Demonstration Page


Half adder schematic

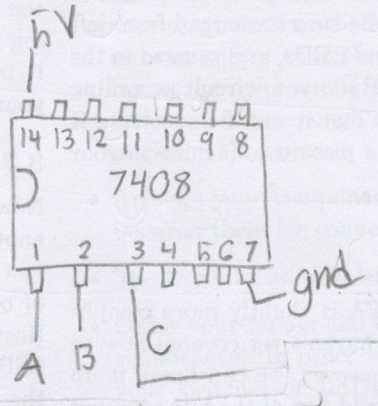



Half adder wiring diagram

Half adder: 

Full adder schematic

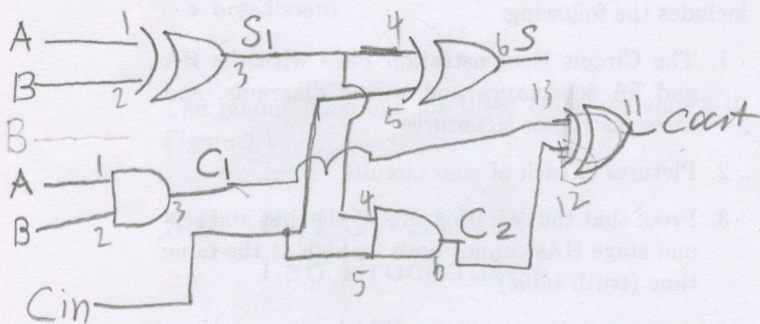

Full adder wiring diagram

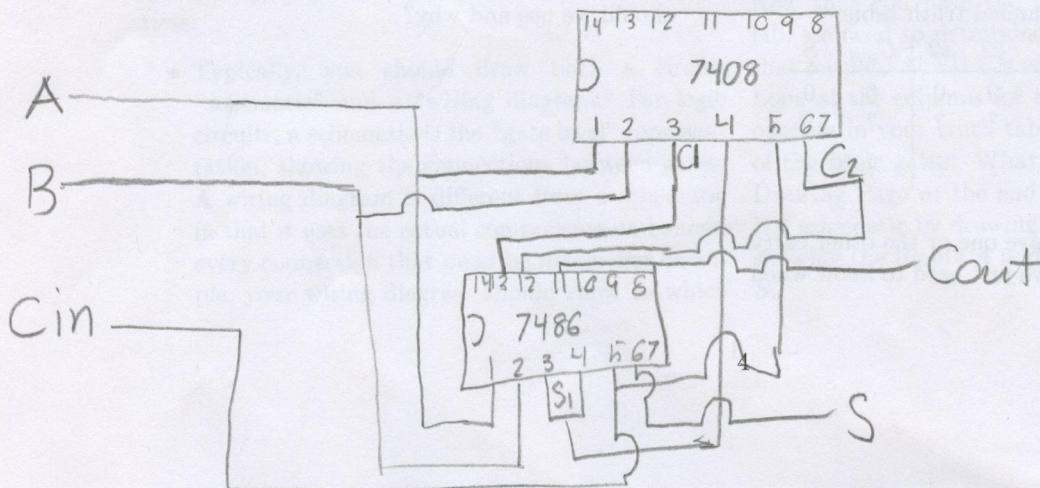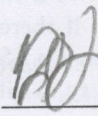Full adder: 2-bit adder: 